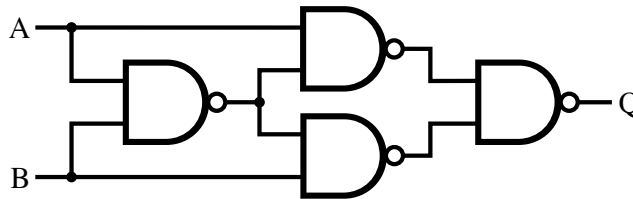


# Neural Networks Assignment (CS1104)

---

## Model 1


This model consist of only NAND gates arranged in suitable order. Below shows the logic diagram of the circuit.



This network executed all the 4 test cases in **0.036s**, with error of 0%.
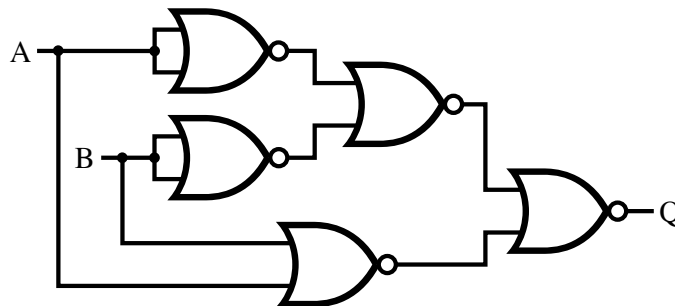
## Model 2


This model consist of only NOR gates arranged in suitable order. Below shows the logic diagram of the circuit.



This network executed all the 4 test cases in **0.003s**, with error of 0%.
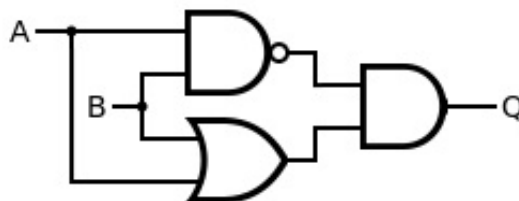
## Model 3

This model consist of NAND, AND and OR gates arranged in suitable order. Below shows the logic diagram of the circuit.



This network executed all the 4 test cases in **0.003s**, with error of 0%.

## How to run

---

```
$ g++ main.cpp --std=c++11  
$ ./a.out
```